

Lecture 2. Diode Models and Circuits (Part 2)


Jaeha Kim

Seoul National University

jaeha@snu.ac.kr

Design of Diode Circuits

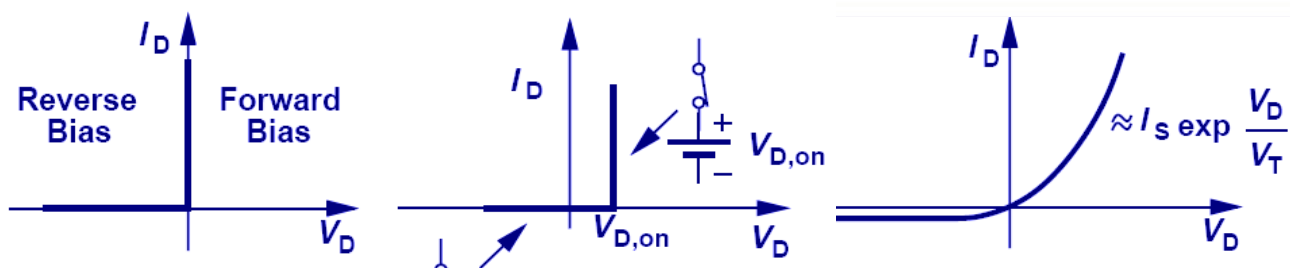- ❑ The ideal diode model is usually sufficient to design circuits and understand functionalities
- ❑ Use more detailed models for analyzing their limitations in reality






Applications of Diode

- ☐ Rectifiers
- ☐ Limiting/clamping circuits
- ☐ Level shifters
- ☐ Track-and-hold switches



Half-Wave Rectifier with R Load

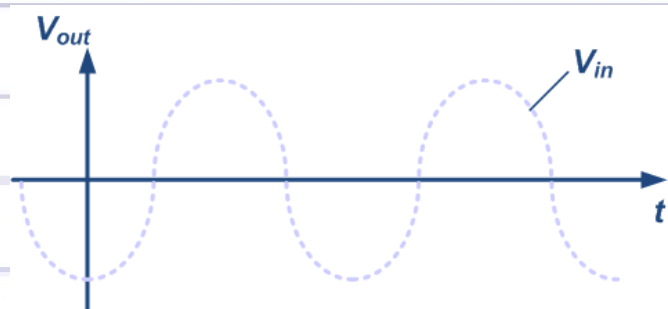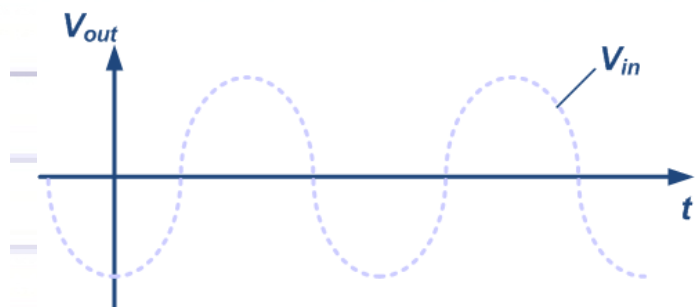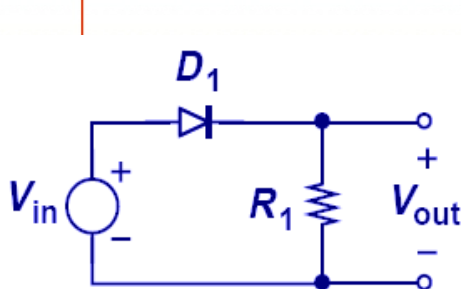- ☐ Draw V_{out} waveforms assuming ideal and constant-voltage models:





Half-Wave Rectifier with C Load

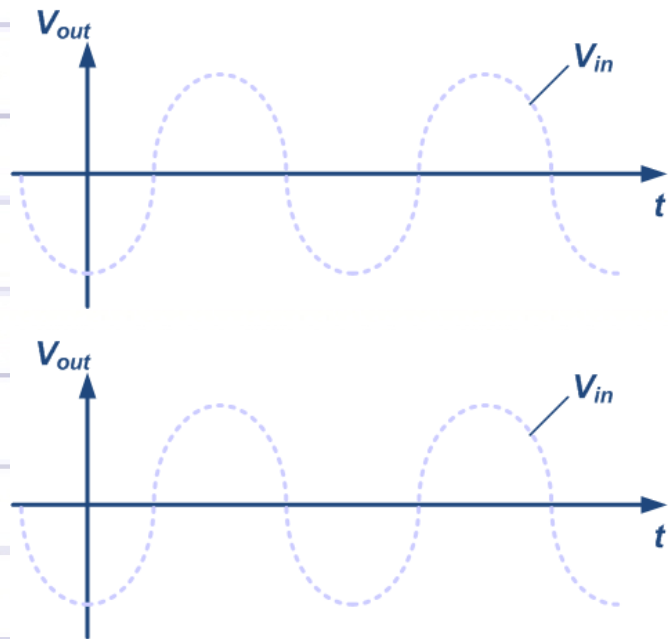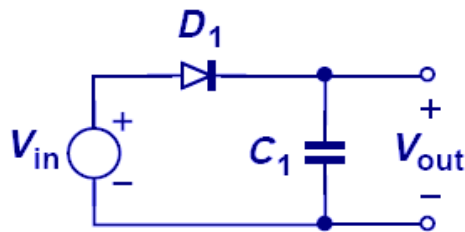- Repeat for a diode driving a capacitor instead of a resistor:




Half-Wave Rectifier with R+C Load

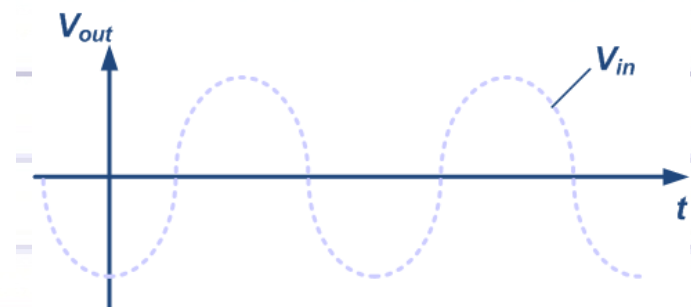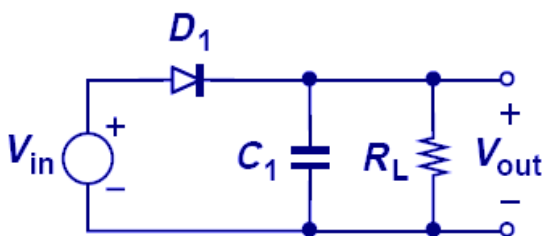- What about when R_L is of finite value?





Half-Wave Rectifier Questions

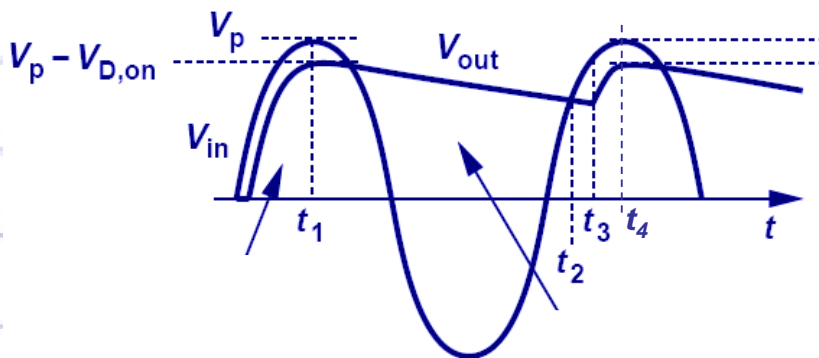- ☐ During which interval the diode is conducting?
- ☐ What is the amount of V_{out} discharge (=voltage ripple)?
- ☐ When does the diode current reach its maximum?




Half-Wave Rectifier Questions (2)

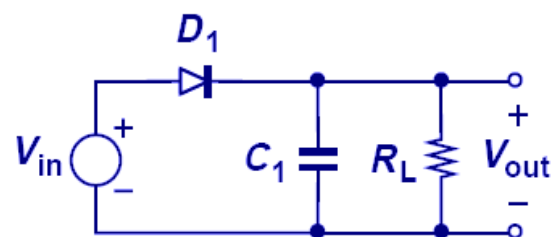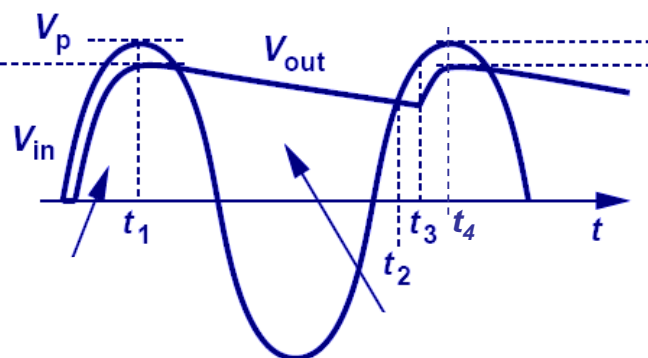- ☐ When does the diode current reach its maximum?




Full-Wave Rectifier

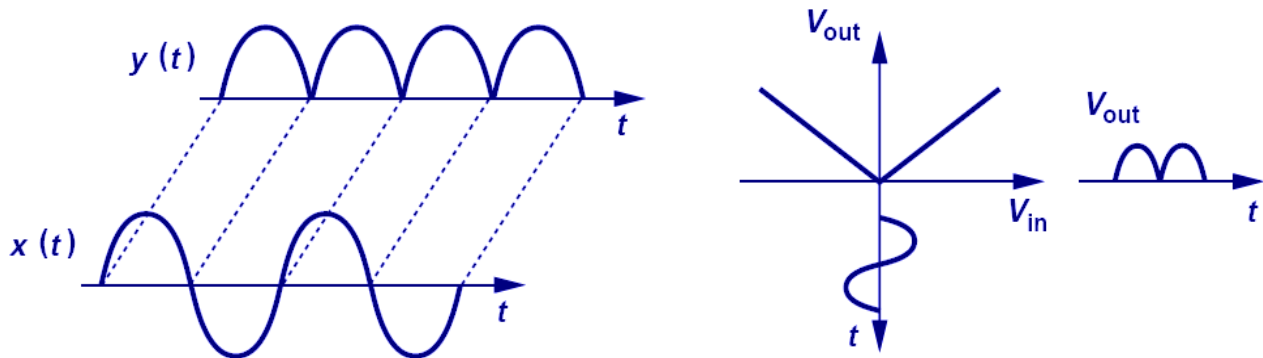- ❑ Throwing out a half of the input energy seems wasteful; can we realize a I/O-curve like below?







Full-Wave Rectifier

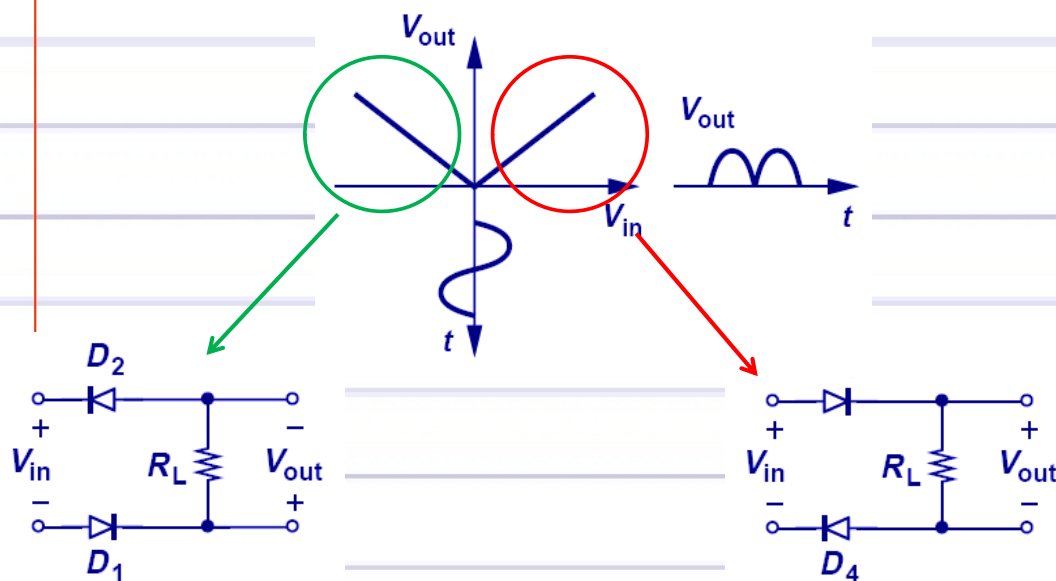


- ❑ Can we combine these two circuits into one?

Bridge Rectifier

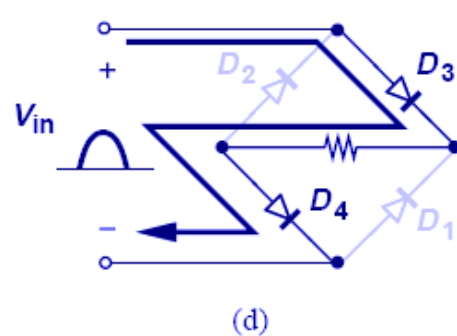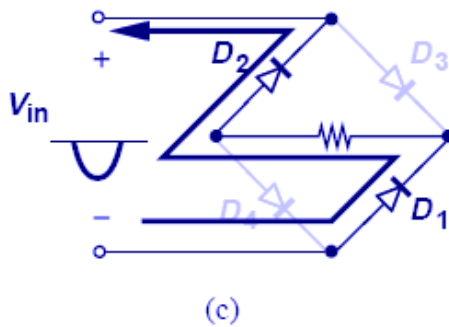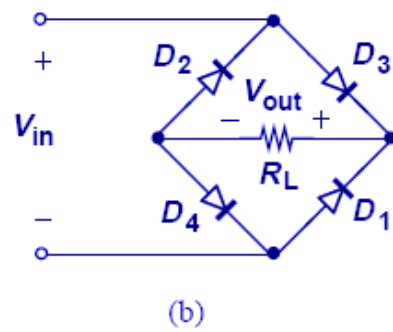
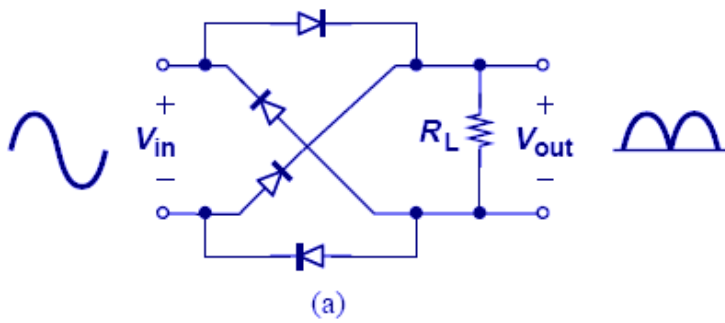


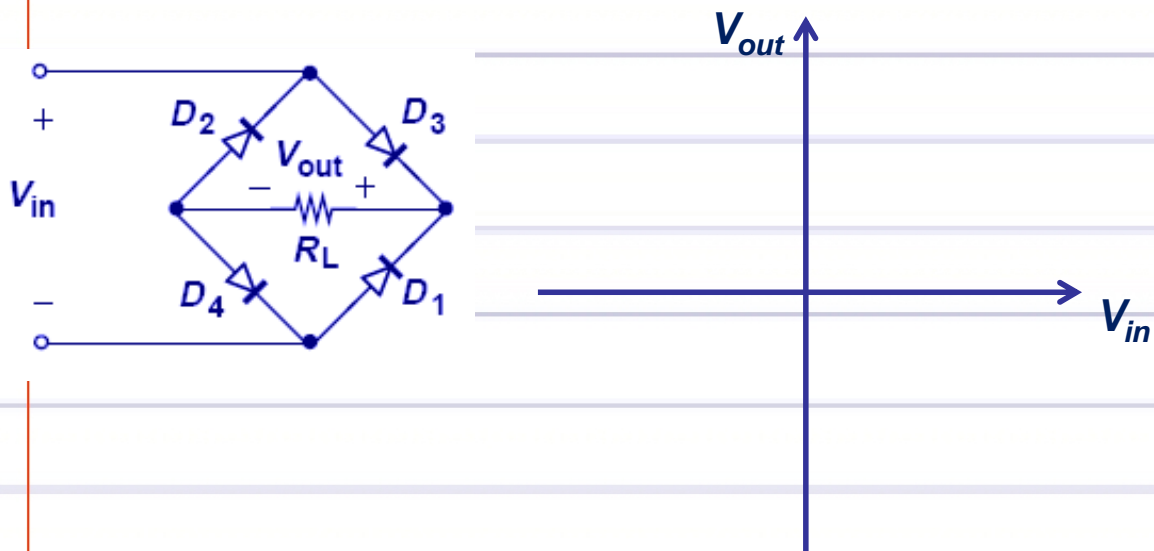Example 3.29



- Plot the I/O characteristic of a full-wave rectifier assuming a constant-voltage model



Half-Wave vs. Full-Wave Rectifiers

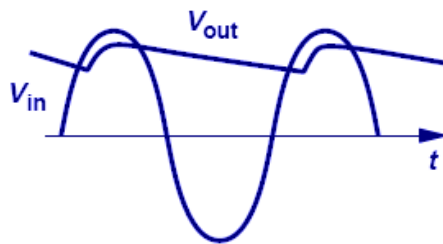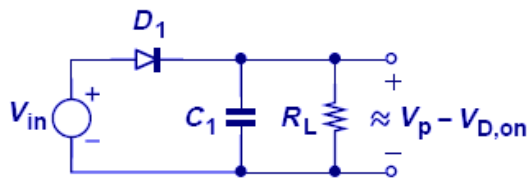


Reverse Bias $\approx 2V_p$

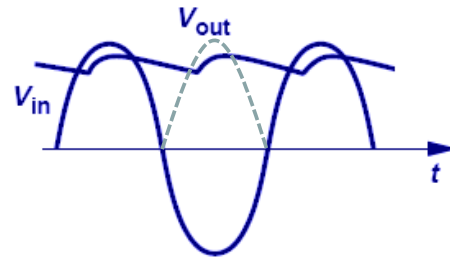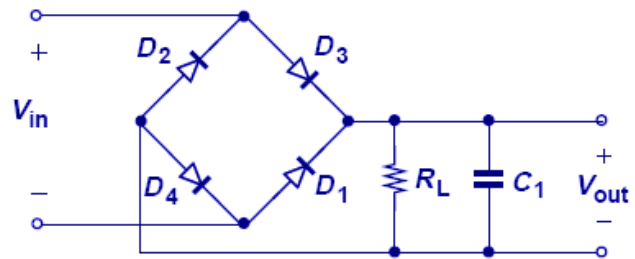

Reverse Bias $\approx V_p$


Limiting Circuits

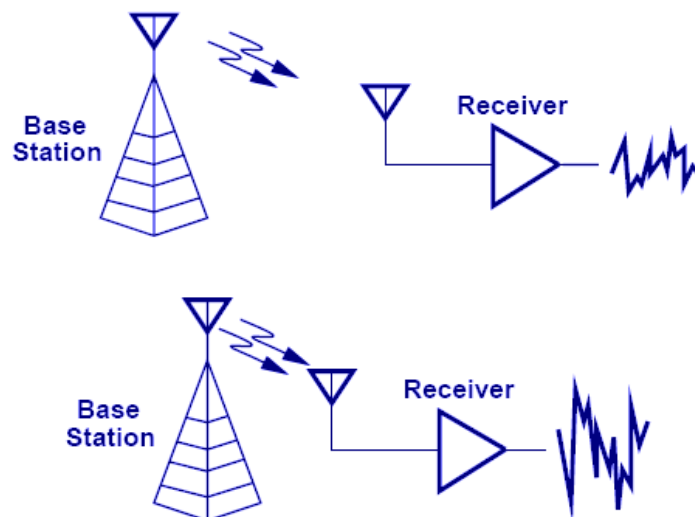- Sometimes, there is a need to limit the maximum amplitude of the input signal




Desired I/O Characteristics

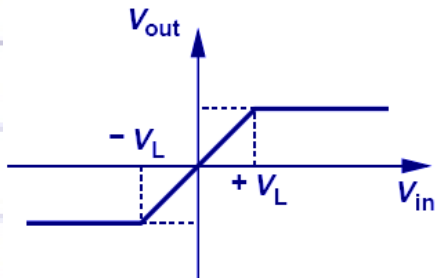□ How would you realize this with diodes?





(a)

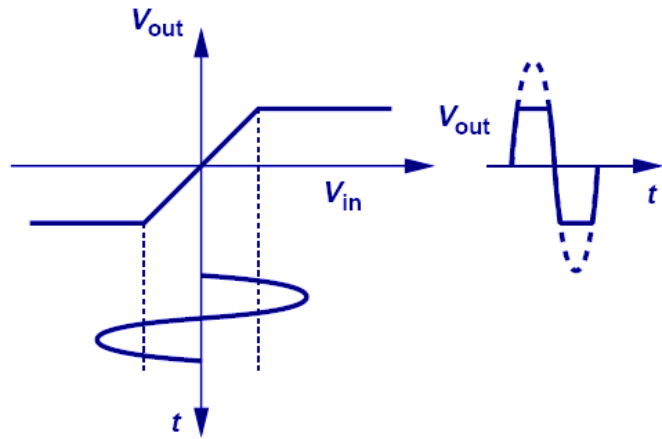

(b)


Limiting Circuit (1)

□ Start with a negative-clipping circuit

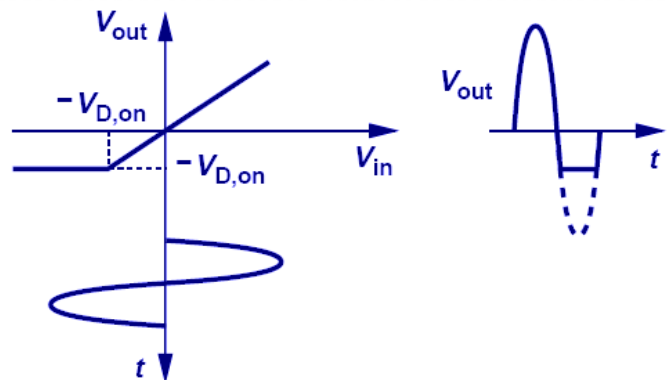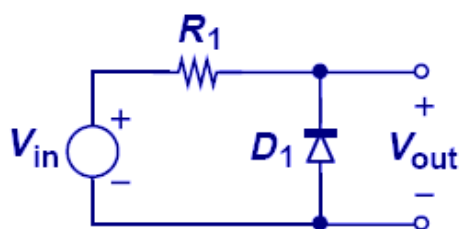


Limiting Circuit (2)

- And add a positive-clipping diode

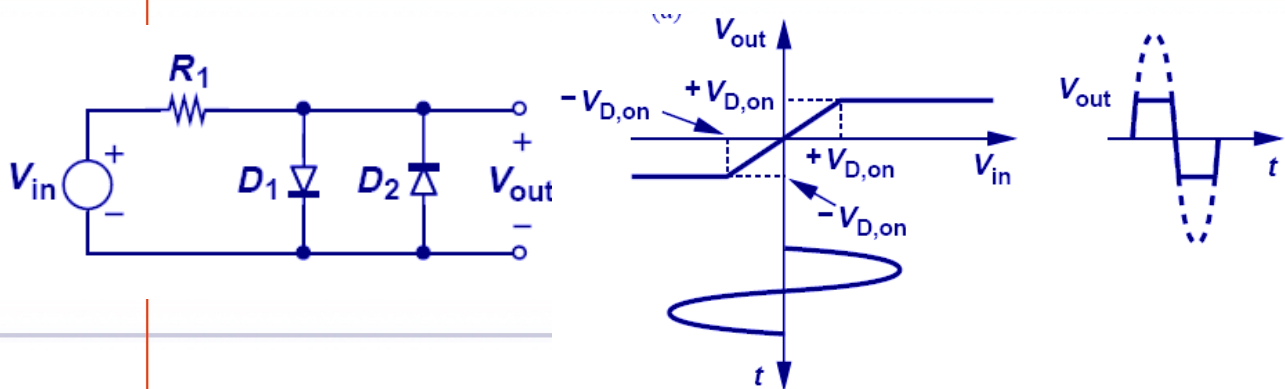


- How can we change the voltage limits?

General Voltage Limiting Circuit

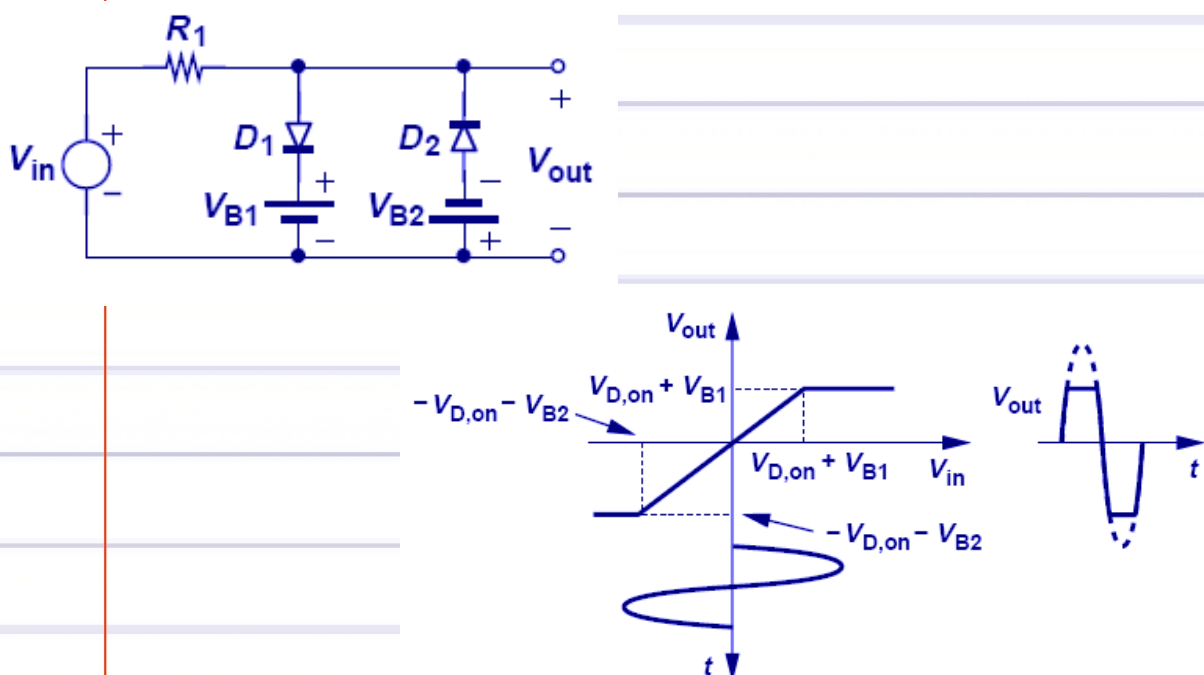


Waveform Shifter

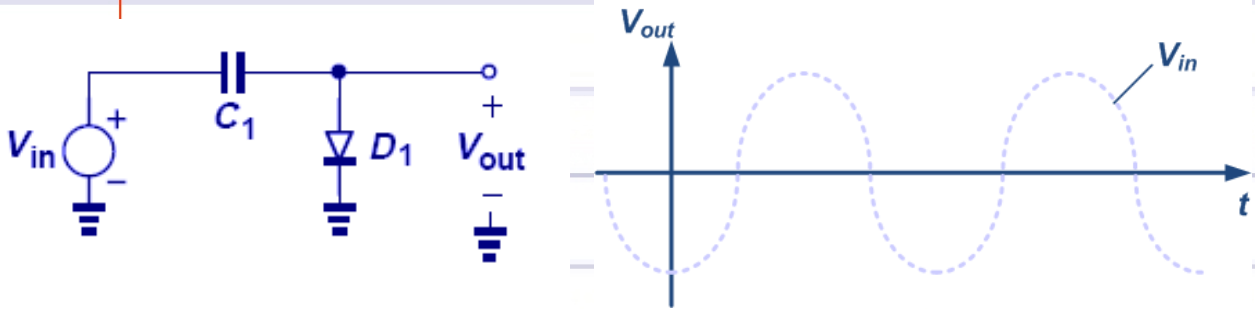- For a sinusoidal V_{in} ($=V_p \cos \omega t$), what is the final voltage across C_1 ?
 - And, what is the relationship between V_{in} & V_{out} ?




Waveform Shifter (2)

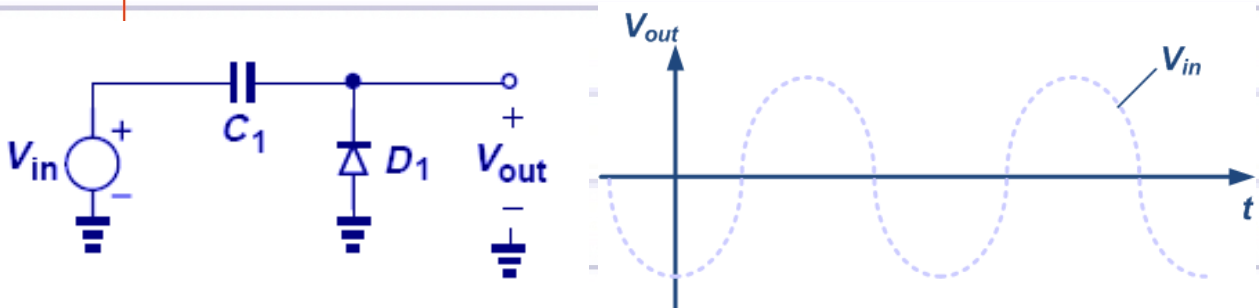- What happens now when the diode is flipped?




Voltage Doubler

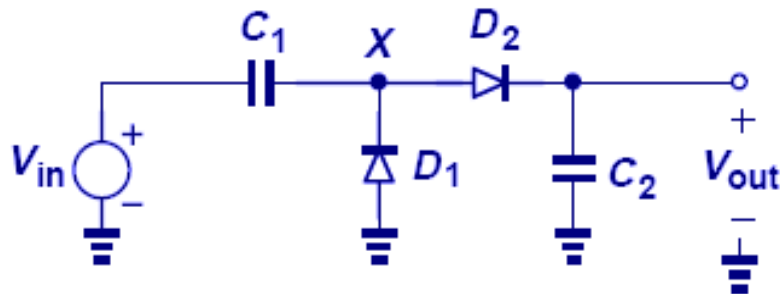□ $V_{in} = V_p \cos \omega t$, what is the final voltage for V_{out} ?




□ For details on transient behaviors, see the text

Voltage Shifter

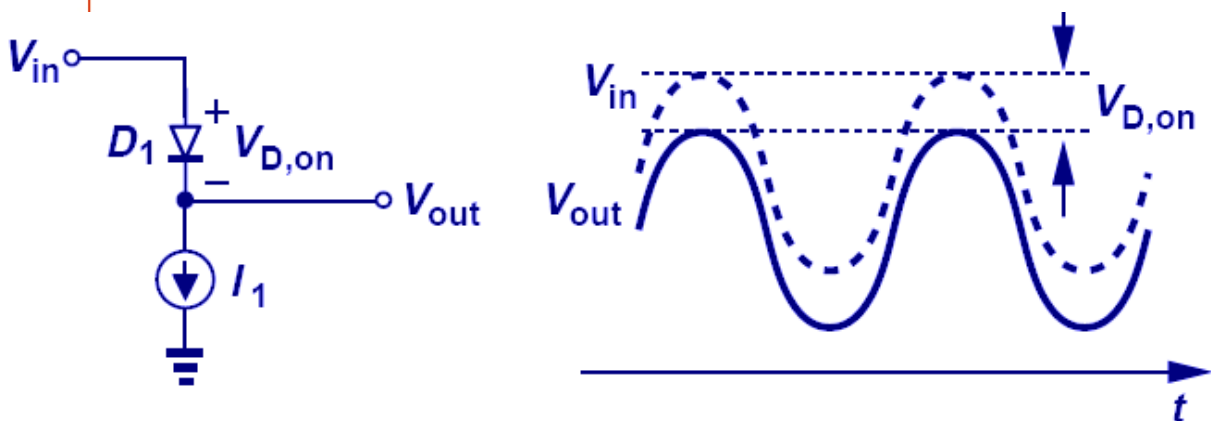


□ What is the model that reflects the design intent?

Voltage Shifter (2)

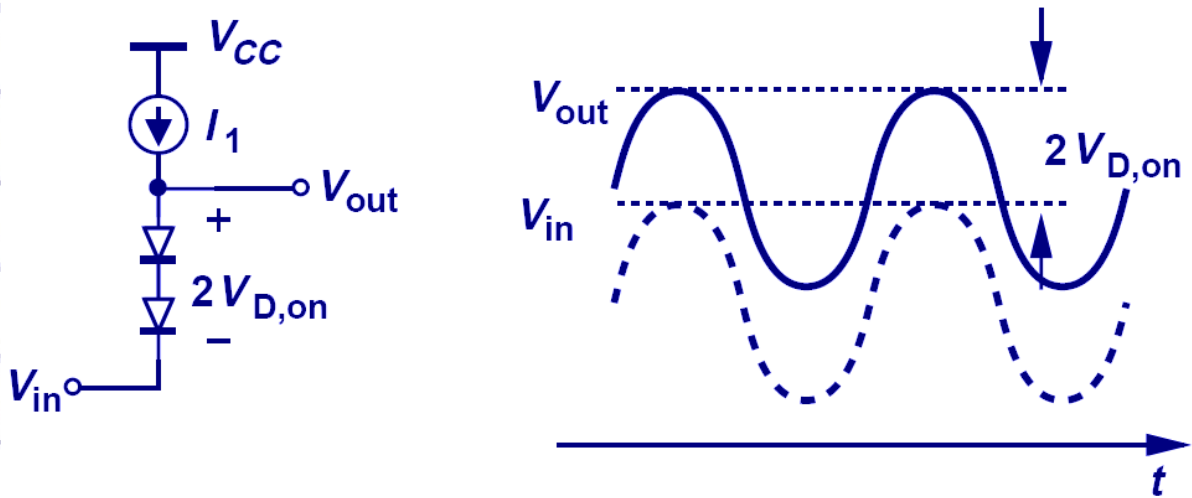


Diode as Switch

- Want to build this using diode:

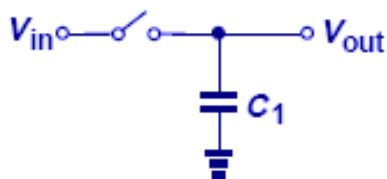


“Track-and-Hold”


- Will this circuit work?

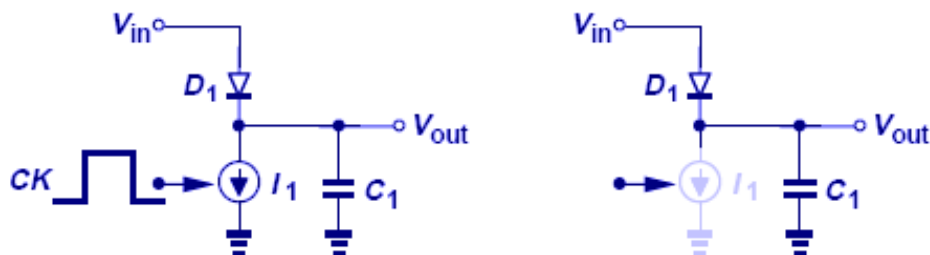

Diode as Switch (2)

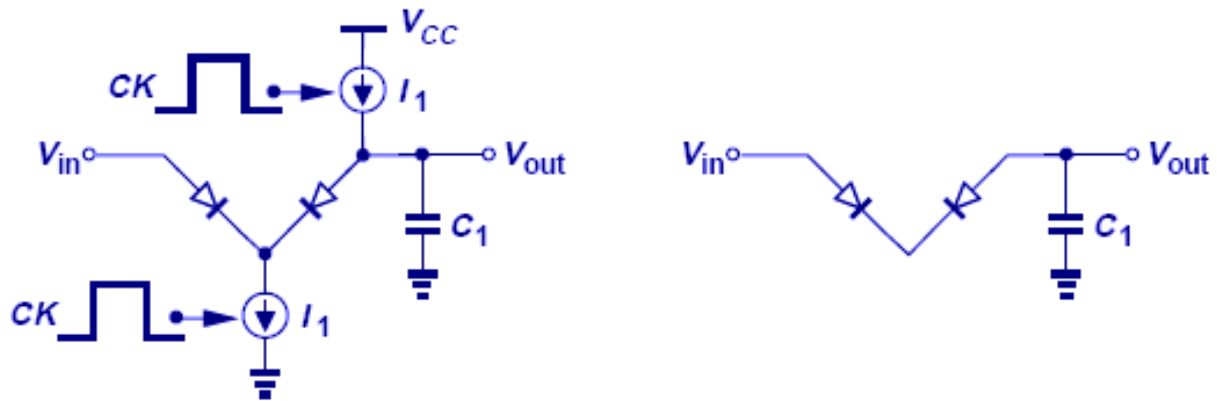

Diode Bridge T&H Switch

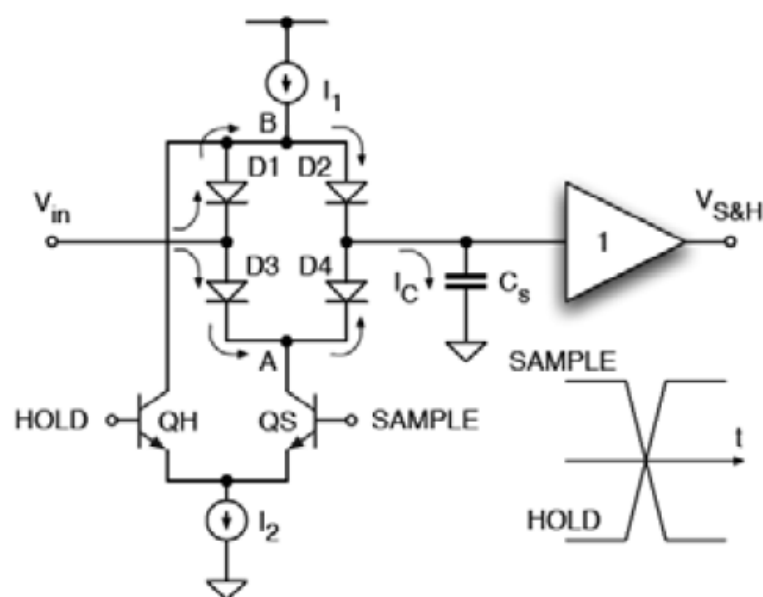

❑ Used for multi-GHz sampling in BJT technologies